


18/03:

UNIT-II:

MULTI STAGE AMPLIFIERS:

* If we increase the stage of the amplifier, then bandwidth ^{or} gain of the amplifier increases.

cascaded/multi-stage.

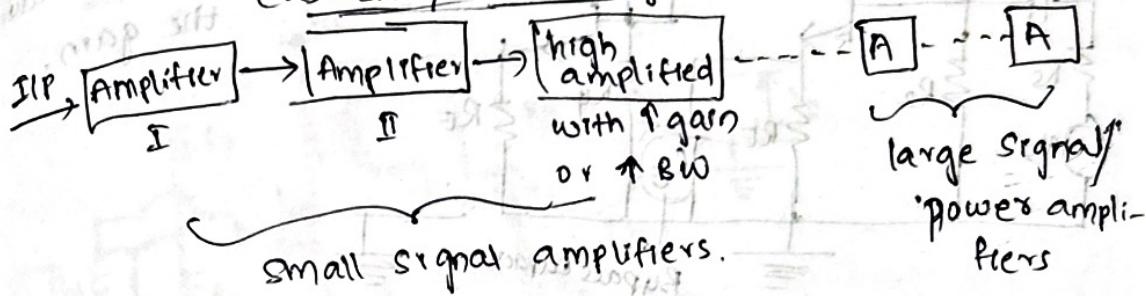

* RC NW are coupling capacitors.

* For a faithful amplification an amplifier should possess,

- i) desired current gain
- ii) desired voltage gain

iii) should match impedance with the source

iv) should match o/p impedance with the load.

* Bcoz of limitations of transistor parameters, the primary requirements of the amplifier are not achieved. Hence more than 1 amplifier stages are cascaded, such that IIP and o/p stages provide impedance matching, and the intermediate stages provide required amplification.

* There are different types of coupling elements that can be employed for cascading the stages of the amplifiers. This is called inter stage coupling.

Methods of interstage coupling:


(1) RC coupling

(2) Transformer coupling

(3) Direct coupling


(4)

IV) RC Coupling: [CE-CE]

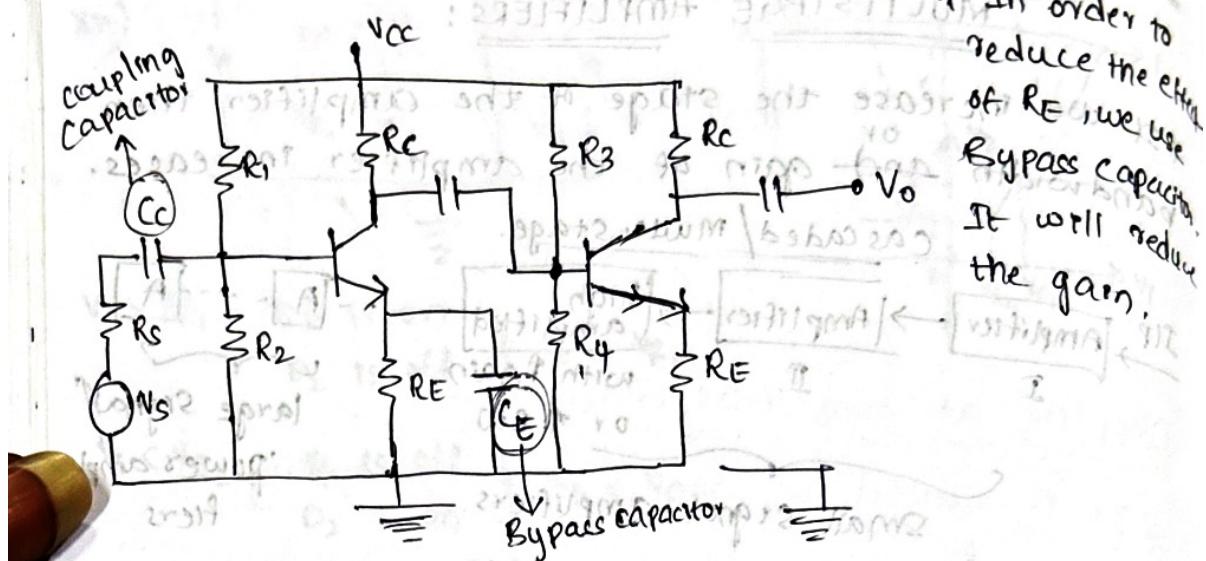

* The o/p of the first stage is coupled to the i/p of the 2nd stage through a coupling capacitor & resistive load at the o/p of the 1st stage.

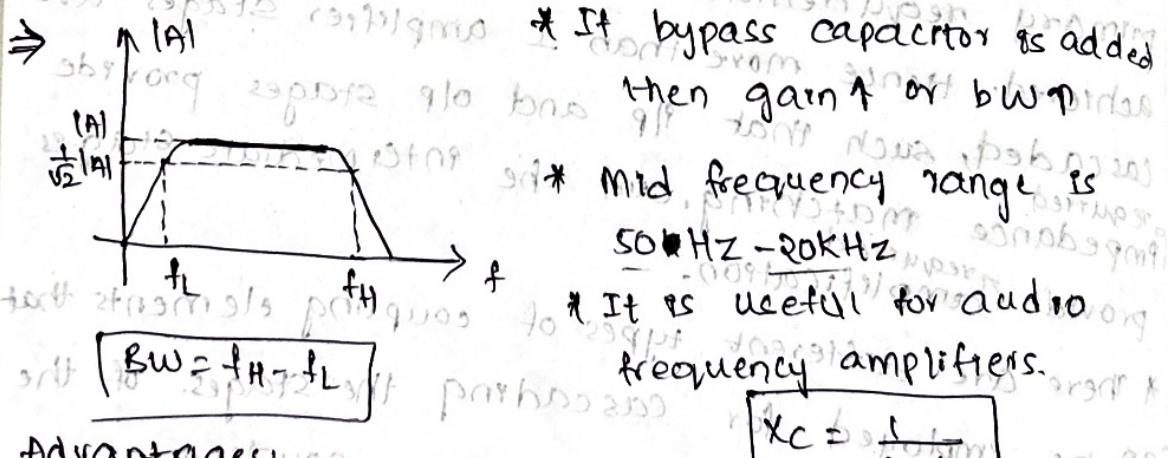* The coupling doesn't effect the Quiescent pt of the next stage, AS, "Cc" bcoz the coupling capacitor "Cc" blocks the dc voltage of 1st stage from reaching the base of the 2nd stage.



Advantages:

- 1) Low cost
- 2) Space required is less
- 3) Almost provides the constant gain in mid frequency range.

Disadvantages:


- 1) Small gain bcoz of loading effect of next stage
- 2) Poor impedance matching.
- 3) Becomes noisy as time passes.

Applications:


- 1) Audio frequency amplifiers
- 2) In early stages of Public addressing systems.
- 3) In tape recorders, TV, CD players.

Transformer coupling: [CE-CE]

(2)

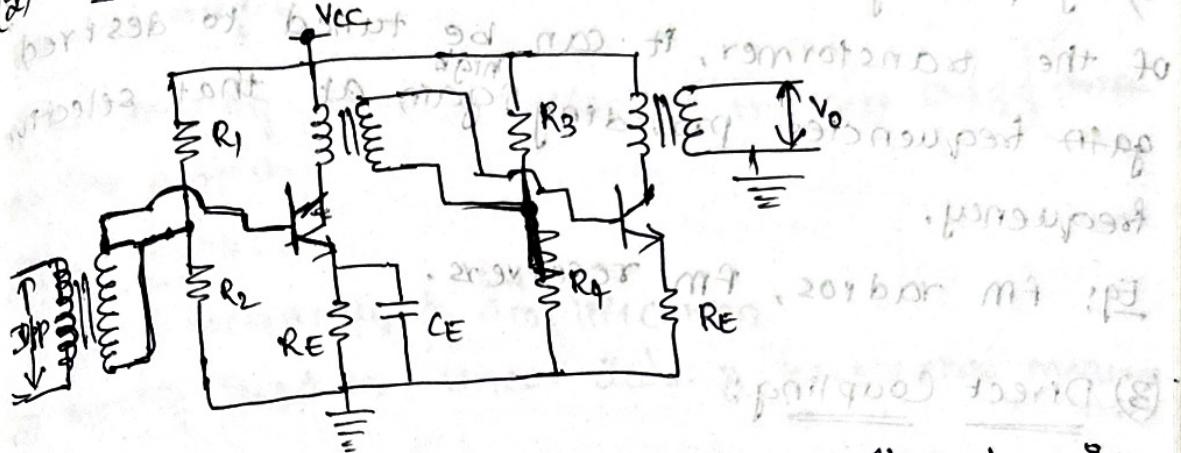

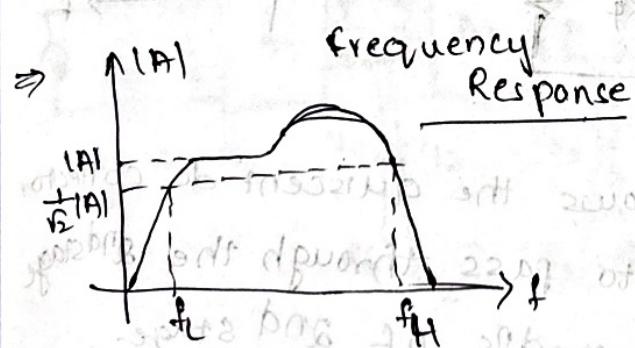* The 1st stage is coupled to next stage through a step-up transformer used to match larger impedance matching transformer used to match larger load resistance of A.F amplifier to a low impedance load like loudspeaker.



* The frequency response is poor for RC coupling bcoz of leakage inductance & inter-winding capacitance will not allow to amplify the signals in different frequency.

Advantages:

- 1) High gain is obtained by step-up coupling transformer.
- 2) No signal power is lost, as DC resistance of primary has less value.

Disadvantages:


- 1) Large in size
- 2) Costlier, as inductances are used.
- 3) Provides poor frequency response.

Applications:

- 1) Used in power amplification.
- 2) Used for amplification of radio frequencies in range of 500KHz to 1600KHz.
- 3) By putting shunt capacitors across each winding of the transformer, it can be tuned to desired gain frequencies providing ^{high} gain at that selective frequency.

Eg: fm radios, fm receivers.

(3) Direct Coupling:

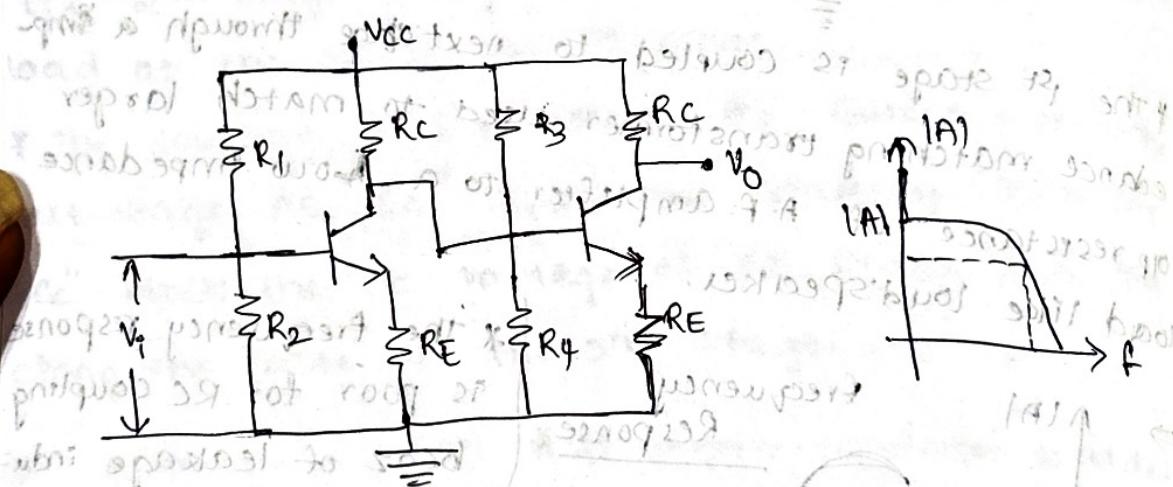

The direct coupling allows the quiescent dc collector current of 1st stage to pass through the 2nd stage affecting the biasing cond's of 2nd stage.

* The low frequency response is very good. But as frequency increases, the shunt and stray capacitances reduce the gain of the amplifier.

* Transistor parameters such as V_{BE} & β changes with temperature causing I_C & V_{CE} to change.

which appears at the base of the next stage producing an unwanted output.

This is called drift.

Advantages:

- 1) Good frequency response at low frequency
- 2) DC amplification can be achieved
- 3) Simple & low cost


Disadvantages:

- 1) DC biasing effects effecting the next stage drift at the output.

Applications:

- 1) Low frequency & amplification.
- 2) Mostly used in linear IC's & bioelectric measurements.

stage cascaded amplifier: ~~2M~~

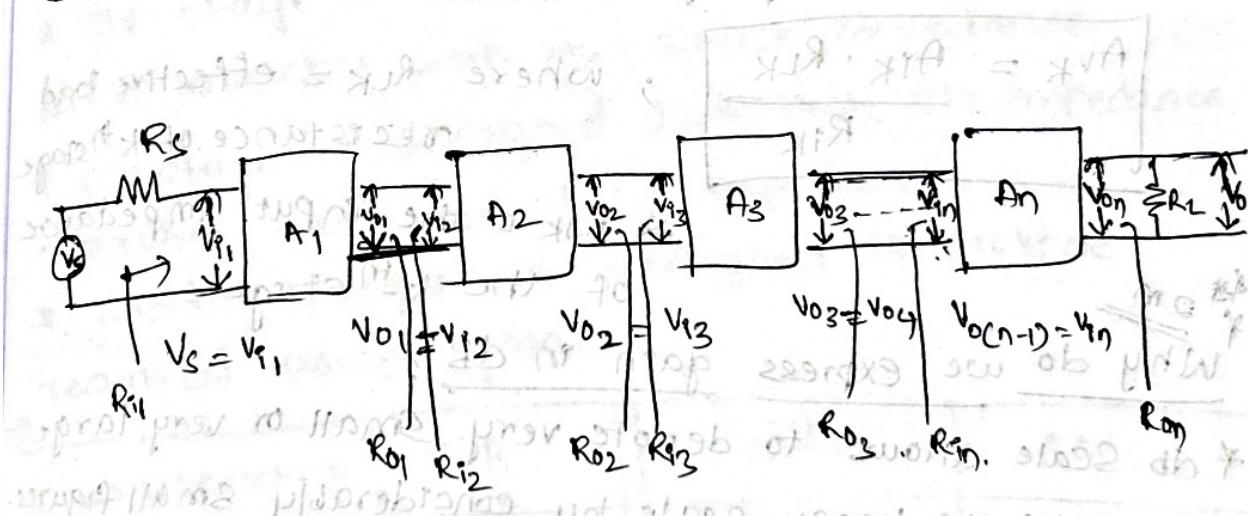

* Cascading means ~~arranging~~ arranging of objects in series (or) sequences. $A_{V1}, A_{V2}, A_{V3}, \dots, A_{Vn}$ are loaded voltage gains.

* The load for 1st Amplifier stage is, R_{I2} .

* The load for 2nd stage is " R_{I2} " & so on.

Consider a 2 stage amplifier ~~A₁ A₂~~

* Overall voltage gain, $A_{V1} = \frac{V_{O1}}{V_{I1}}$

$A_{V2} = \frac{V_{O2}}{V_{I2}} = \frac{V_{O2}}{V_{O1}}$

$$A_{VS} = \frac{V_{O2}}{V_{I1}}$$

$$= \frac{V_{O2}}{V_{I1}} \times \frac{V_{I1}}{V_{I2}}$$

$$A_{VS} = A_{V2} \cdot A_{V1}$$

* The total voltage gain is the product of individual voltage gains.

* Similarly, for an N -Stage Amplifier;

$$A_{VS} = A_{V1} \cdot A_{V2} \cdot A_{V3} \cdots A_{Vn}$$

for k^{th} stage, Voltage gain is,

$$A_{VK} = \frac{A_{VK} \cdot R_{LK}}{R_{IK}}$$

; where R_{LK} = effective load resistance of k^{th} stage

& R_{IK} is the input impedance of the k^{th} stage.

Why do we express gain in dB?

* db Scale allows to denote very small or very large quantities of linear scale by considerably small figures

* Sound heard by human ear response to sound intensities on logarithmic scale rather than linear scale

Hence db is more appropriate to represent amplifier gains.

* It is convenient to compare 2 powers in logarithmic scale rather than linear scale. The unit of logarithmic scale is decibels. It can be generally represented as

$$N(\text{dB}) = 10 \log \frac{P_2}{P_1}$$

P_2 → 10P power

P_1 → 1P power.

$\text{dP} \rightarrow$ represents power ratio

Garn of Multistage Amplifier in dB:

The overall gain of a multi-stage amplifier in dB is the sum of decimal voltage gains of the individual stages.

$$\therefore \text{AVT(dB)} = A_{V1}(\text{dB}) + A_{V2}(\text{dB}) + \dots + A_{Vn}(\text{dB})$$

Selection of configuration in a cascaded amplifier:

Basically multi-stage amplifier is divided into 3 stages:

i) IIP stage

ii) intermediate/middle stage

iii) OLP stage:

* IIP stage is designed such that its IIP impedance matches with the source impedance.

* OLP stage is designed such that OLP impedance matches with the load impedance.

* middle stages are designed to provide required power gain.

characteristics	CB	CE	CC
IIP impedance	very low (20Ω)	100Ω ($1\text{ k}\Omega$)	($10\text{k}\Omega$) high
OLP resistance	very high ($1\text{ M}\Omega$)	high ($10\text{k}\Omega$)	low (50Ω)
current gain	less than 1	high	high
voltage gain	medium	medium	low
applications	used as IIP stage used as initial stage	for audio signal amplification, used as intermediate stage.	used as OLP stage, impedance matching.

Input stage selection:

i) source impedance is low, hence O/P impedance is also low. Then CB amplifier can be used in initial stage.

O/P stage:

We need to drive a very low impedance ~~load~~ ^{load}. Then O/P resistance is ~~totally~~ ^{above} low. It can be provided by CC amplifier.

Intermediate Stage:


which gives better voltage gain & current gain. CE amplifier satisfies both conditions.

Ques:


Q: Calculate R_i , A_{11} , A_V , R_o & A_{VS} & A_{IS} if the ckt parameters are $R_{SS} = 1\text{ k}\Omega$, $R_{C1} = 15\text{ k}\Omega$, $R_{E1} = 100\text{ }\mu\Omega$, $R_{C2} = 4\text{ k}\Omega$, $R_E = 330\text{ }\mu\Omega$, with $R_1 = 200\text{ k}\Omega$ and $R_2 = 20\text{ k}\Omega$ for the 1st stage and $R_1 = 47\text{ k}\Omega$, $R_2 = 4.7\text{ k}\Omega$ for the second stage of CE amplifier with 2 stages with being CE.

Assume, $\beta_{IE} = 1.2\text{ k}\Omega$, $\beta_{FE} = 50$, $\beta_{RE} = 2.5 \times 10^{-4}$, $\beta_{OE} = 2.5 \times 10^4$.

Sol:

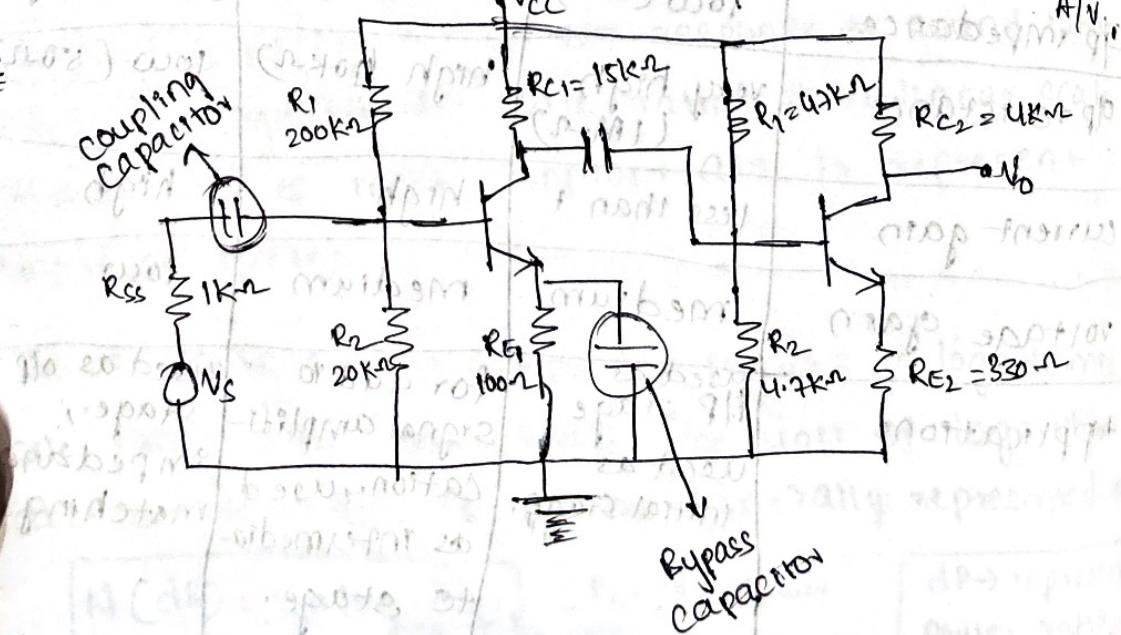

Step-1): Draw the H-parameter model

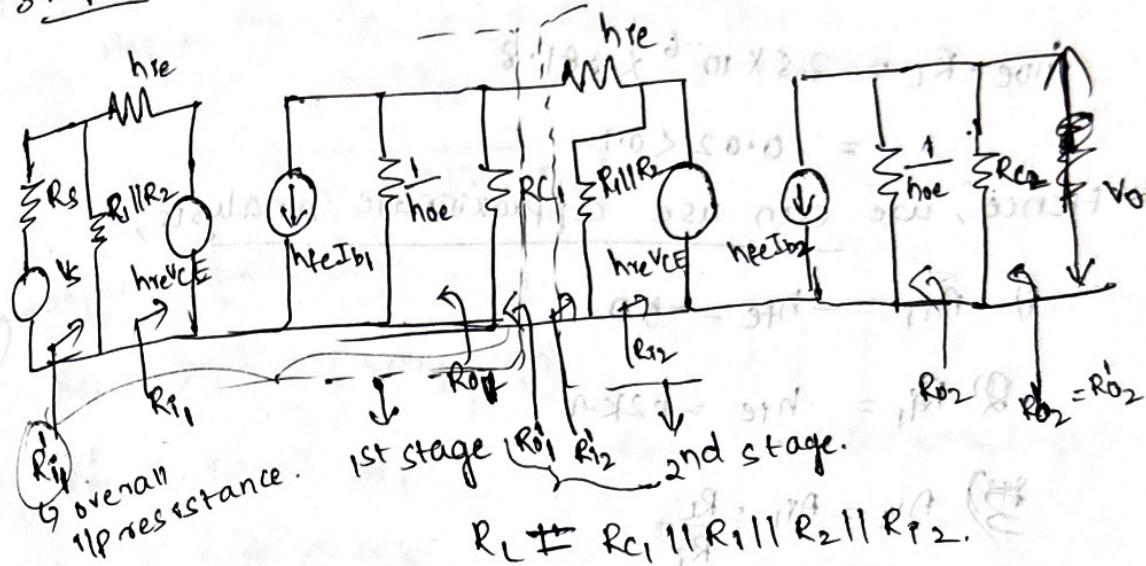

Step-2): To analyze the stages.
Always start the analysis with the 2nd stage then the 1st stage.

Analysis of 2nd stage: $h_{fe} R_L < 0.1$

For approximate analysis, $R_L = R_C$

$$f_{A2} = -h_{fe} = -50$$

$$R_{L2} = h_{re} = 1.2k\Omega$$

$$f_{AV2} = f_{A2} \times \frac{R_L}{R_{L2}}$$

$$[R_L = R_C]$$

$$f_{AV2} = -50 \times \frac{4 \times 10^3}{1.2 \times 10^3} = -166.66$$

Analysis of 1st stage:

$$R_L = R_C \parallel R_1 \parallel R_2 \parallel R_{L2}$$

$$= 1.5k \parallel 4.7k \parallel 4.7k \parallel 1.2k$$

$$= 1.5k \parallel \frac{4.7k \parallel 4.7k}{1.2k}$$

$$= \frac{176250}{53} \parallel 1.2k \quad [1.2k \approx 2V/A]$$

$$R_L = 881.8 \Omega$$

$$h_{oe} - R_L = 25 \times 10^{-6} \times 881.8 \\ = 0.02 < 0.1$$

Hence, we can use approximate analysis,

1) $A_{V1} = -h_{fe} = -50$

2) $R_{p1} = h_{re} = 1.2 \text{ k}\Omega$

3) $A_{V1} = A_{V1} \cdot \frac{R_L}{R_{p1}}$

$$= -50 \cdot \frac{881.8}{1.2 \times 10^3}$$

$A_{V1} = -36.74$

4) Gain of two stages,


$$A_{VT} = A_{V1} \cdot A_{V2}$$

$$= (-166.66)(-36.74)$$

$A_{VT} = 6123.0884$

$A_{VT} = 2500$

5) Overall voltage gain,

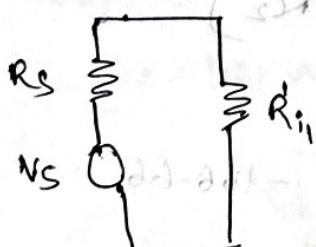

$$R_{p1}' = R_1 || R_2 || R_1$$

$$\text{for } X_F = 200k || (20k) || 1.2k$$

$$= 18.18k || 1.2k$$

$|R_{i1}'| = 1.1257k$

6) $A_{VS} = A_{V1} \cdot \frac{R_{p1}'}{R_s + R_{p1}'}$

$$= (6123.0884) \cdot \frac{1.1257k}{1.1257k + 1.2k}$$

$A_{VS} = 3242.58$

1) overall current gain,

$$A_{IS} = A_P \cdot \frac{R_S}{R_S + R'_I} = 2500 \cdot \frac{1K}{1K + 14257K}$$

$$A_{IS} = 1176.08$$

2) output resistance:

$$R_O = 25M\Omega \text{ (very high)}$$

$$R'_O = R_O \parallel R_C \\ = \infty \parallel 15K \\ = 15K\Omega$$

$$R'_O = 15K\Omega$$

$$R_O = 25M\Omega \text{ (Very high)}$$

$$R'_O = R_O \parallel R_C \\ = \infty \parallel 4K \\ = 4K\Omega$$



$$R'_O = 4K\Omega$$

\Rightarrow Expressions for A_i , R_i , A_v , R_o , R_{ot} using approximate h-model

Quantity	CE	CB	CC
A_i	$-h_{fe}$	$\frac{h_{fe}}{1+h_{fe}}$	$1+h_{fe}$
R_i	h_{ie}	$\frac{h_{ie}}{1+h_{fe}}$	$h_{ie} + (1+h_{fe})R_L$
A_v	$h_{fe} \cdot \frac{R_L}{h_{ie}}$	$h_{fe} \cdot \frac{R_L}{R_E}$	$1 - \frac{h_{ie}}{R_p}$
R_o	∞	∞	$\frac{h_{ie} + R_S}{1+h_{fe}}$
R_{ot}	R_L	R_L	$R_O \parallel R_L$

23/03:

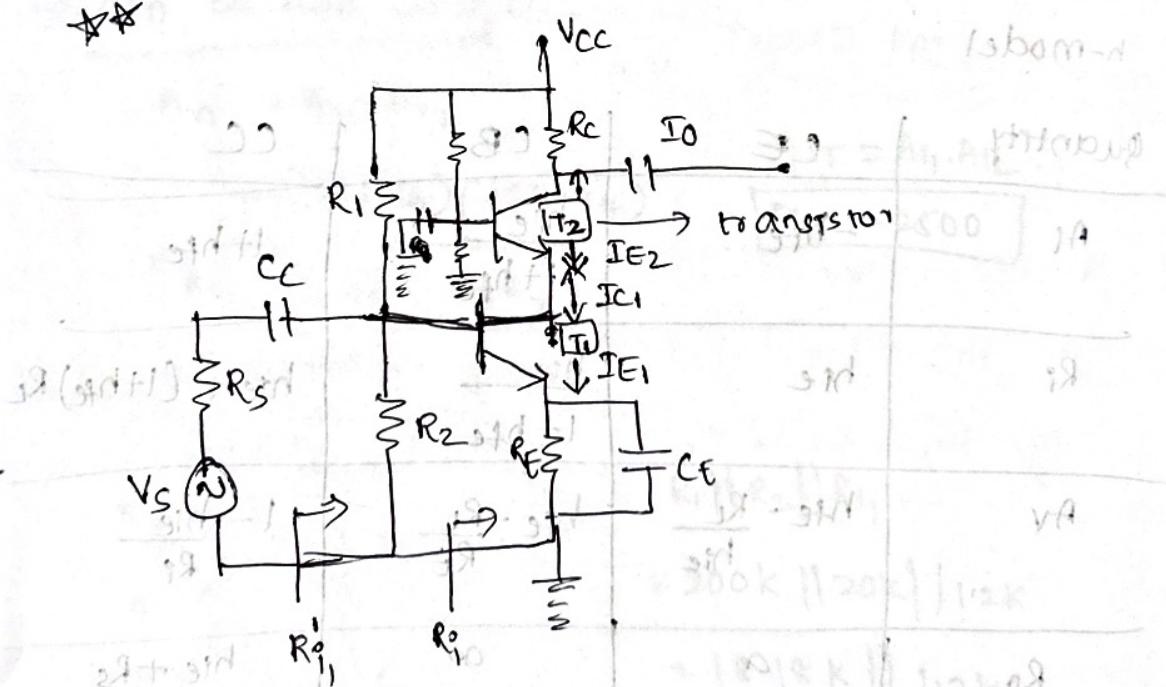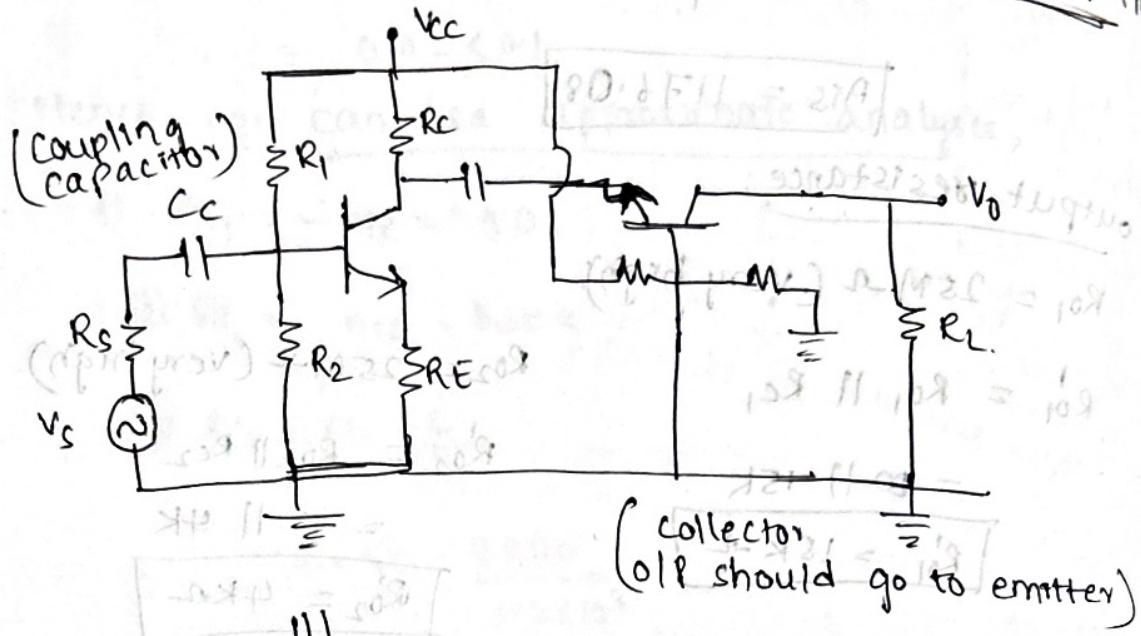Combination of CE & CB Amplifier / CASCADE Amplifier



→ CE amplifier acts as input stage and CB amplifier acts as output stage. A cascode amplifier consists of a CE amplifier in series with a CB amplifier.

→ It is a approach to solve the low impedance problem of CB amplifier.

→ I_E for T_1 is by V_{E1} & R_{E1} ,

$$I_{E1} = \frac{V_{E1}}{R_{E1}}$$


$$\Rightarrow I_{C1} = I_E$$

I_{E2} is same as I_C , [$I_{E2} = I_{C1}$]
we know that; $I_{E2} \approx I_{C2}$

$$I_{C2} \approx I_E$$

∴ The current remains constant regardless of level of V_{BG} as long as V_{EE_1} is large enough for the current operation of T_1 .

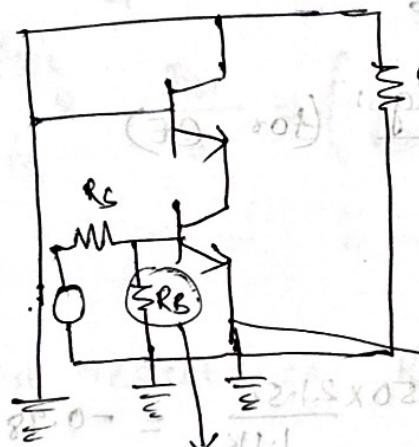
AC Equivalent circuit for Cascode Amplifier:



As ~~bias~~ bypass capacitor shorted, no resistance

parallel combination
of R_1 & R_2

H-parameter model of Cascode Amplifier:

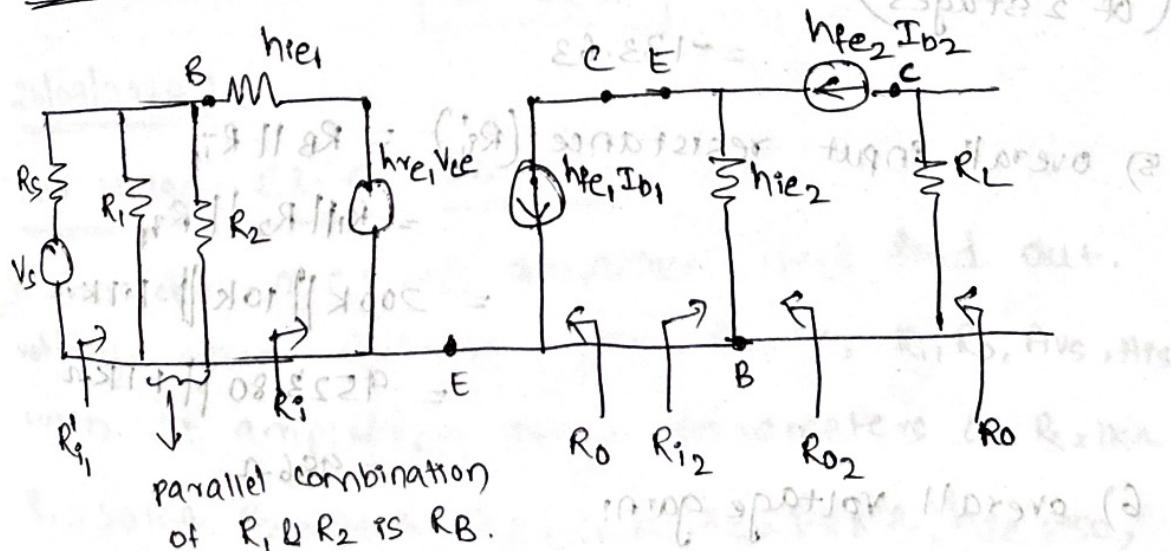

Consider the circuit parameters $R_S = 1\text{ k}\Omega$, $R_1 = 200\text{k}\Omega$, $R_2 = 10\text{k}\Omega$, $R_L = 3\text{k}\Omega$. Transistor parameters for both transistors are $h_{ie} = 1.1\text{k}\Omega$, $h_{fe} = 50$

Analysis of the second stage:

$$1) A_{12} (\text{current gain}) = \frac{h_{fe}}{1+h_{fe}} \quad (\text{for CB}) \\ = 0.98$$

$$2) R_{12} = \frac{h_{ie}}{1+h_{fe}} = 21.56 \Omega$$

$$3) A_{v2} = A_{12} \times \frac{R_L}{R_{12}} \\ = 0.98 \times \frac{3 \times 10^3}{21.56} = 136.36$$

Analysis of the 1st stage:

(for CE)

$$1) A_{11} = -h_{fe} = -50$$

$$2) R_{11} = h_{ie} = 1.1 \text{ k}\Omega$$


$$3) A_{v1} = A_{11} \times \frac{R_L}{h_{ie}} = -50 \times \frac{21.56}{1.1 \text{ k}} = -0.98$$

$$4) A_{VT} \\ (\text{voltage gain of 2 stages}) = A_{v1} \times A_{v2} \\ = -0.98 \times 136.36 \\ = -133.63$$

$$5) \text{overall input resistance } (R_{i1}) = R_B \parallel R_{11}$$

$$= R_1 \parallel R_2 \parallel R_{11} \\ = 200 \text{ k} \parallel 10 \text{ k} \parallel 1.1 \text{ k} \Omega \\ = 9523.80 \parallel 1.1 \text{ k} \Omega$$
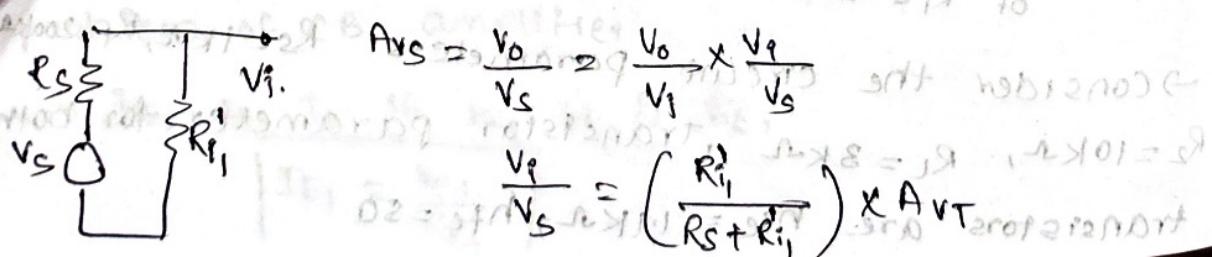
$$6) \text{overall voltage gain: } = 986 \Omega$$



$$A_{VS} = \frac{V_o}{V_s} = \frac{V_o}{V_1} \times \frac{V_1}{V_s}$$

$$\frac{V_1}{V_s} = \left(\frac{R_{11}}{R_s + R_{11}} \right) \times A_{VT}$$

$$= \left(\frac{986}{1 \times 10^3 + 986} \right) \times (-133.63)$$


$$= -66.34$$

7) $A_{VS} = \frac{I_0}{I_S} = \frac{I_0}{I_{C2}} \times \left(\frac{I_{C2}}{I_{E2}} \right) \times \frac{I_{E2}}{I_{C1}} \times \left(\frac{I_{C1}}{I_{E1}} \right) \times \frac{I_{E1}}{I_S}$

$\downarrow A_{I_2}$ $\downarrow A_{I_1}$ $\downarrow I_{B_1}$ \downarrow find out

$$\Rightarrow \frac{I_0}{I_{C2}} = -1 \quad \hookrightarrow \text{opp. dire}$$

$$\frac{I_{E2}}{I_{C1}} = -1$$

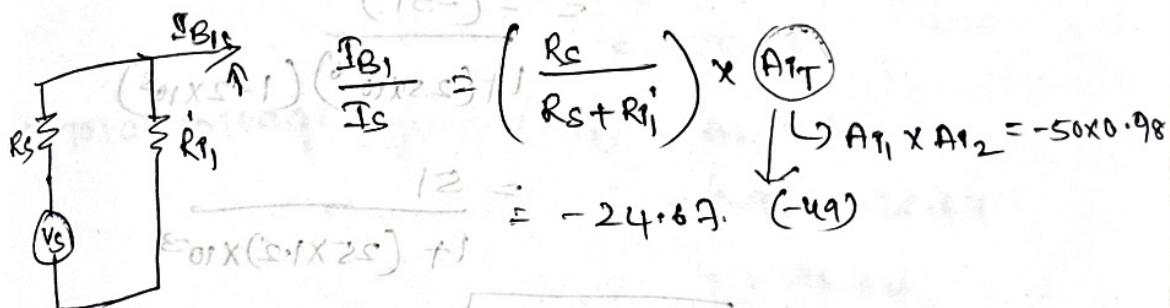

8) output resistance $R_O = \infty$ $\begin{cases} R_{O1} = \infty \\ R_{O2} = \infty \end{cases}$

$$\therefore R_O = R_{O2} \parallel R_L$$

$$R_{O2} = \infty \parallel 3k\Omega + 80 \times 10^{-6}$$

$$\boxed{R_O = 3k\Omega}$$

26/03/2024:

Two stage CE-CC Amplifier:


Q) Consider a CE-CC amplifier and find out voltage gain, current gain, A_V , A_1 , R_i , R_o , A_{VS} , A_{PS} with CE amplifier stage parameters as $R_S = 1k\Omega$

$R_1 = 50k\Omega$, $R_2 = 2k\Omega$, $R_C = 1k\Omega$, $R_L = 1.2k\Omega$, $h_{FE} = 80$,

$h_{ie} = 2k$, $h_{oe} = 25mA/V$, $h_{re} = 6 \times 10^{-4}$ and for CC

amplifier the transistor parameters are $h_{ic} = 2k$

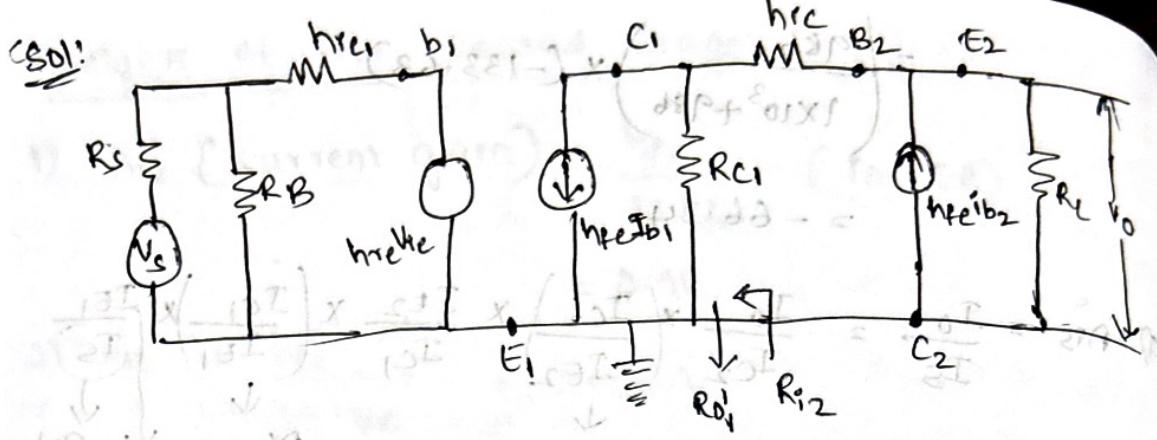$h_{tc} = -51$, $h_{rc} = 1$, $h_{oc} = 25mA/V$ (go exact analysis)



Analyses of 2nd stage CC Amplifier:

1) Current gain (A_{I2}) = $\frac{-h_{fc}}{1 + h_{oc}R_L}$

$$= \frac{-(-51)}{1 + (25 \times 10^{-3})(1 - 2 \times 10^3)}$$

$$= \frac{51}{1 + (25 \times 1.2) \times 10^{-3}}$$

$$A_{I2} = 49.5$$

2) $R_{I2} = h_{ic} + h_{rc} \times A_{I2} \times R_{e2}$
 $= 2 \times 10^3 + 1 \times 49.5 + 1.2 \times 10^3 \quad (R_L = R_{e2})$

$$R_{I2} = 61.4 \text{ k}\Omega$$

3) Voltage gain (A_{V2}) = $A_{I2} \times \frac{R_L}{R_{I2}}$

$$(49.5) \times \frac{1.2 \times 10^3}{61.4 \times 10^3}$$

$$A_{V2} = 0.96$$

(Voltage gain is less than 1)

Analyses of 1st stage:

1) Net load resistance (R_{o1}) = $R_{C1} // R_{I2}$

$$\approx 1 \text{ k}\Omega // 61.4 \text{ k}\Omega$$

$$= \frac{(61.4 \text{ k})(1 \text{ k})}{(1 + 61.4) \times 10^3} = 1 \text{ k}\Omega \text{ (approx)}$$

$$3) A_{11} (\text{current gain}) = \frac{-h_{fe}}{(1+h_{fe}) R_{o1}} = -48.78$$

$$3) \text{Input impedance } (R_{i1}) = h_{ic} + h_{re} A_{11} - R_{o1}$$

$$= 2 \times 10^3 + (6 \times 10^{-4})(-48.78)(1 \times 10^3)$$

$$= 1.9 \text{ k}\Omega$$

$$4) \text{Voltage gain } (Av_1) = A_{11} \times \frac{R_{o1}}{R_{i1}}$$

$$= -48.78 \times \frac{1 \times 10^3}{1.9 \times 10^3}$$

$$= -25.67$$


$$5) \text{Total voltage gain } (Av_T) = Av_1 \times Av_2$$

$$= 0.96 \times -25.67$$

$$= -24.64$$

$$6) \text{Overall voltage gain } (Av_S) = \frac{V_o}{V_S} = \frac{V_o}{V_{i2}} \times \frac{V_{i2}}{V_{i1}}$$
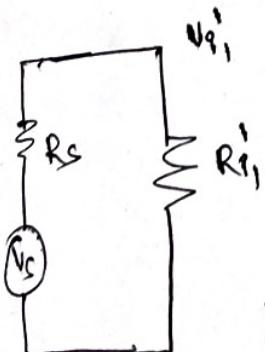
$$= Av_2 \times Av_1 \times \frac{V_{i1}}{V_S}$$



$$R_{i1}' = R_1 || R_2 || R_{i1}$$

$$\therefore \left[\frac{V_{i1}}{V_S} = \frac{R_{i1}'}{R_S + R_{i1}'} \right]$$

$$= \frac{Av_2 \times Av_1 \times R_{i1}'}{R_S + R_{i1}'}$$

$$R_{i1}' = 0.95 \text{ k}\Omega$$

$$= 0.96 \times (-25.67) \times 0.95 \text{ k}$$

$$= \frac{0.96 \times (-25.67) \times 0.95 \text{ k}}{1 \text{ k} + 0.95 \text{ k}}$$

$$Av_S = -12.00$$

$$7) \text{Overall current gain } (A_{IS}) = \frac{I_{C2}}{I_S} = \frac{I_{C2}}{I_{B2}} \times \frac{I_{B1}}{I_{C1}} \times \frac{I_{C1}}{I_{B1}} \times \frac{I_B}{I_A}$$


$$= A_{12} \times (-1) \times A_{11} \times \frac{R_s}{R_{i1} + R_s} \quad (\text{Comp. Gain})$$

$$= -A_{12} \times A_{11} \times \frac{R_s}{R_{i1} + R_s}$$


$$= -(49.51)(-48.78) \times \frac{1\text{ k}\Omega}{0.95\text{k} + 1\text{k}}$$

Home Assignment = $+1238.511.$

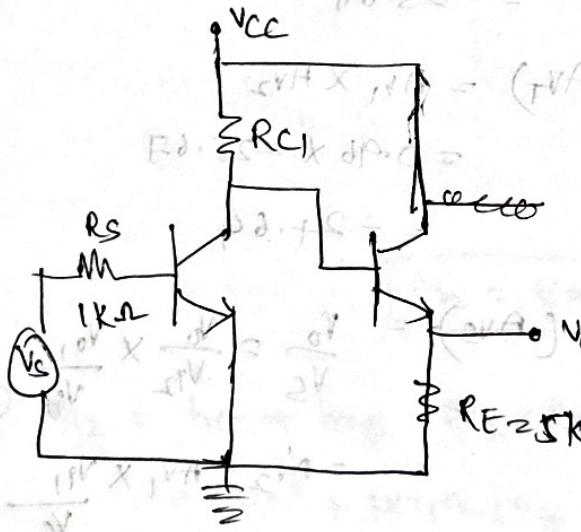Q1) Design a CE-CC Amplifier with $R_s = 1\text{k}\Omega$, $R_{C1} = 10\text{k}\Omega$, $R_E = 5\text{k}\Omega$. Assume $h_{re} = 2\text{k}\Omega$, $h_{rc} = 2\text{k}\Omega$, $h_{fe} = 50$, $h_{oe} = 6 \times 10^{-4}$, $h_{oc} = 1$, $h_{oe} = h_{oc} = 25\text{mA/V}$



Millers Theorem:

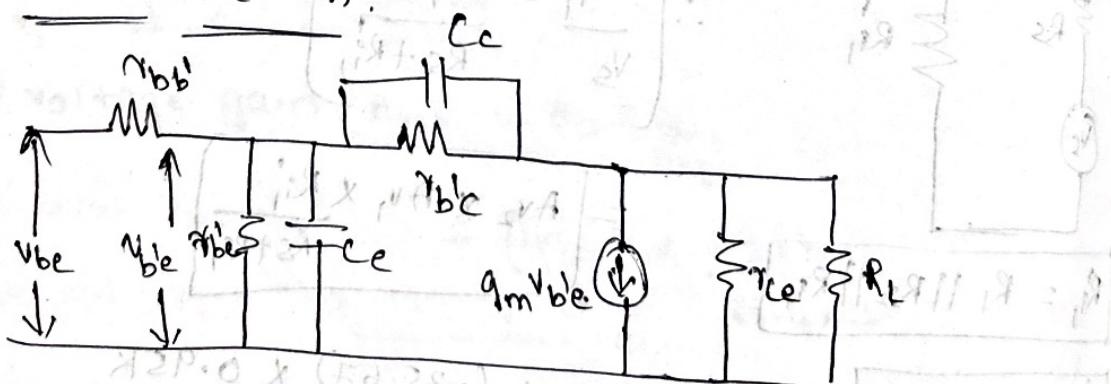


* Short circuit current gain β_c is derived by considering $R_L = 0$ this is required to maintain transistor in active region. This figure shows the CE hybrid

π -model.

- * $Nb'C$ and Ec acting as feedback common to both HP & OP side.
- * when there is an impedance common to both HP & OP using "Miller's theorem" the Z -impedance can be separated to two individual impedances.


Miller's theorem:

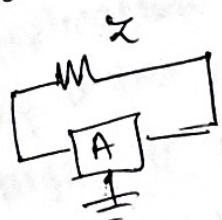consider a circuit where the impedance Z is common to both HP and OP



Then the impedance Z can be separated as Z_1, Z_2

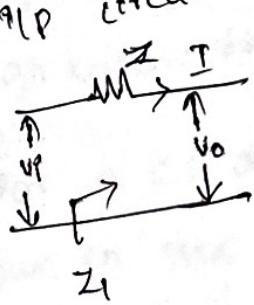The Miller's theorem states that "the effect of HP circuit is the ratio of HP voltage to current".



$$Z_1 = \frac{V_o}{I}$$


$$I = \frac{V_i - V_o}{Z} \Rightarrow Z_1 = \frac{V_i}{\frac{V_i - V_o}{Z}} = \frac{V_i Z}{V_i - V_o}$$

divide N^* & D^* with V_i

$$Z_1 = \frac{Z}{1 - \frac{V_o}{V_i}} \Rightarrow Z_1 = \frac{Z}{1 - K}$$

$$\boxed{Z_1 = \frac{Z}{1 - K}} \quad \left(K = AV = \frac{V_o}{V_i} \right)$$

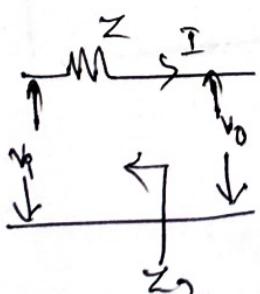Similarly, the effect of resistance at OP circuit is the ratio of OP voltage to current



$$Z_2 = \frac{V_o}{I}$$

$$I = \frac{V_o - V_i}{Z}$$

$$Z_2 = \frac{V_o}{\frac{V_o - V_i}{Z}} \Rightarrow Z_2 = \frac{Z V_o}{V_o - V_i}$$

Divide N' and D' with V_F . profit is $\frac{N'}{V_F}$

$$Z_2 = \frac{Z \cdot V_0}{V_F}$$

$\frac{V_0}{V_F} - 1$ left "minimum voltage" part

$$Z_2 = \frac{Z \cdot A_V}{A_V - 1}$$

$$\boxed{Z_2 = Z \cdot \frac{k}{k-1}}$$

using Miller's theorem,

$$Z_1 = \frac{\gamma b c}{k-1}; \quad C_C(1-k)$$




$$Z_2 = \frac{\gamma b c k}{k-1}, \quad \frac{k}{C_C(k-1)}$$

H-parameters for exact analysis:

$$1) A_{11} = \frac{-h_f}{1+h_{21}}$$

! theore

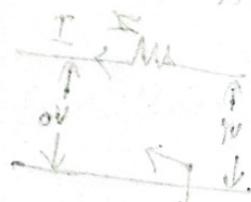

$$2) A_{12} = A_{11} \cdot \frac{R_L}{R_1} \rightarrow \frac{V_2}{V_1} = \frac{R_L}{R_1}$$

$$3) R_{11} = h_{11} + h_{12} A_{11} R_L$$

$$4) R_{12} = \frac{R_L + h_{12}}{h_{11} + h_{12} - h_{11} h_{21}}$$

$$h_{11} R_L + [h_{11} h_{21} - h_{12} h_{11}]$$

From circuit diagram, considering
we expect to maintain transistor
 $V_{DS} = E$, choose the $p-n-p$ hybrid
 $V_{DS} = E$, $\frac{V_{DS}}{V_D} = \frac{V_{DS}}{E}$

Q1: Why CE-CB called Cascode Amplifier:


- If an amplifier comprises of BJT's then the 1st stage is common-emitter configuration that feeds to the common base at which the o/p is collected. This type of amplifier is known as cascode amplifier.


The CB Amplifier is known for wider BW but the low o/p impedance of CB is a limitation for many applications. The solution is to precede the CB stage by a low gain CE stage which has moderately high o/p impedance. (ISCE :-)

It can have different characteristics like high o/p / o/p isolation, high o/p / o/p impedance, high bandwidth.

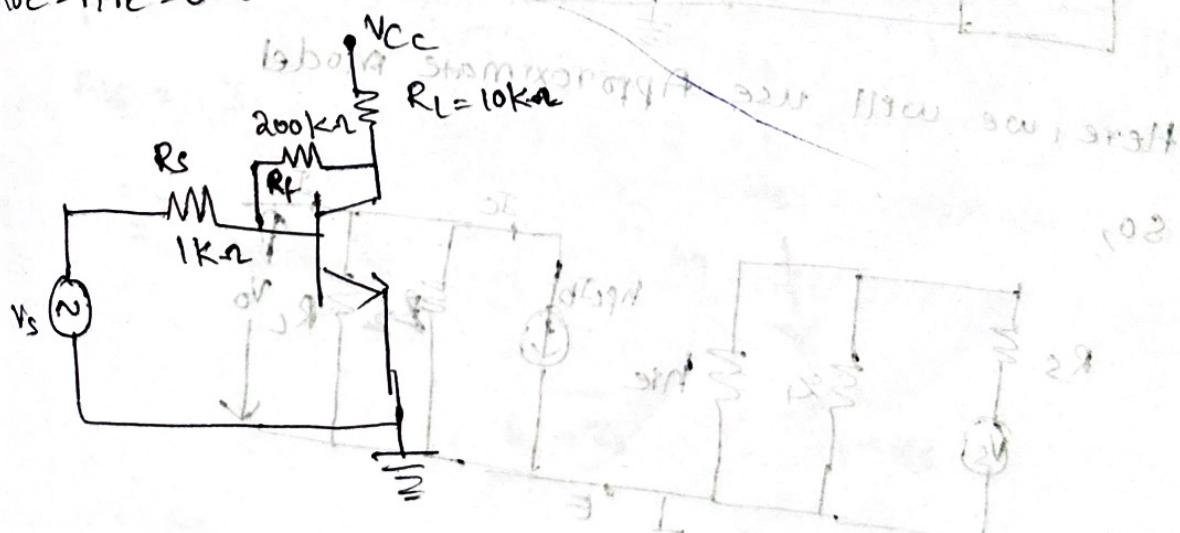Q103:

For a CE amplifier with collector to base bias, shown in the figure, calculate R_i , A_f , A_v , A_{vs} , R_o . The transistor parameters are $h_{ie} = 1.1 \text{ k}\Omega$, $h_{fe} = 50$, $h_{oe} = h_{re} = 0 \text{ n}$



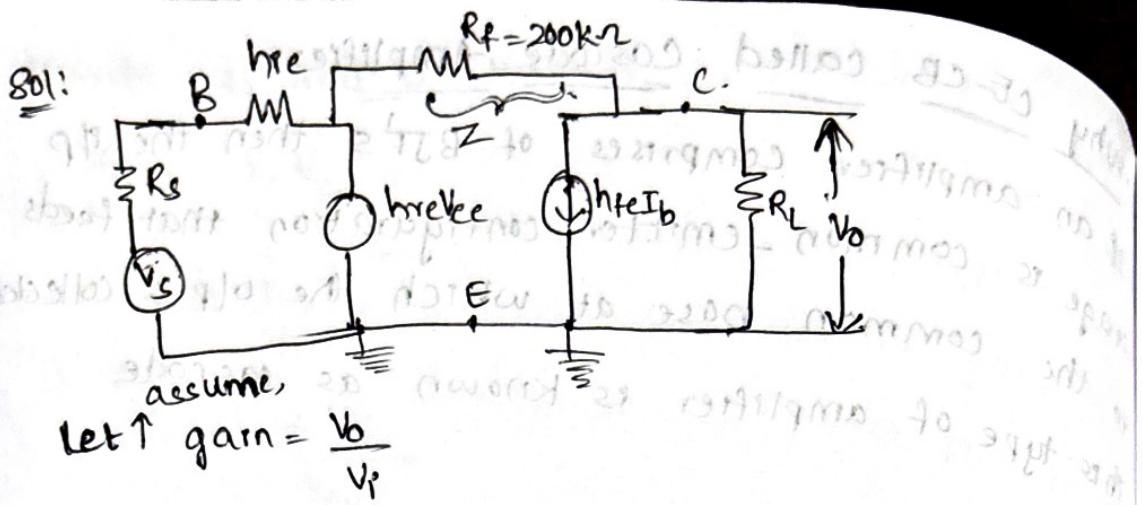


for a CE amplifier,
 $\text{gain} > 1$

$$|A_V(0)| K > 1$$


$$\therefore Z_2 = \frac{Z \cdot K}{K-1} \quad (\because K \gg 1)$$
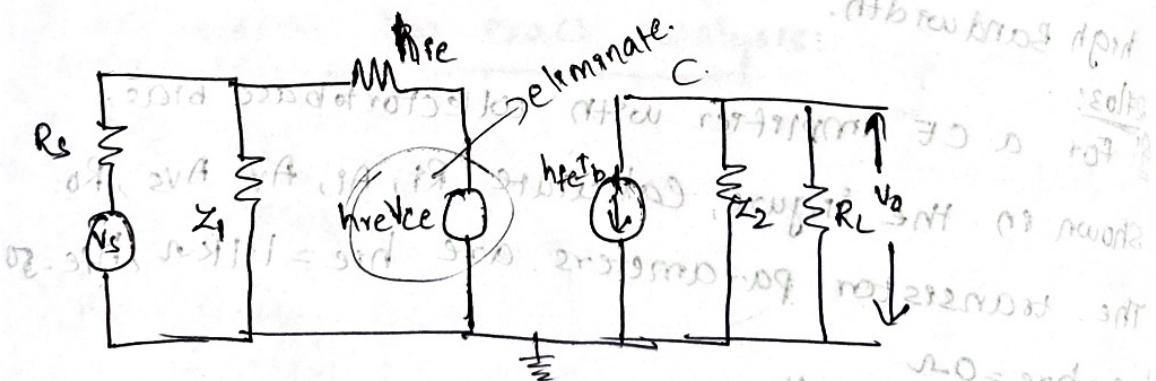
$$\text{since } Z_2 = \frac{Z \cdot K}{K} \Rightarrow Z_2 = Z = 200\text{ k}\Omega$$



Here, we will use Approximate model

so,

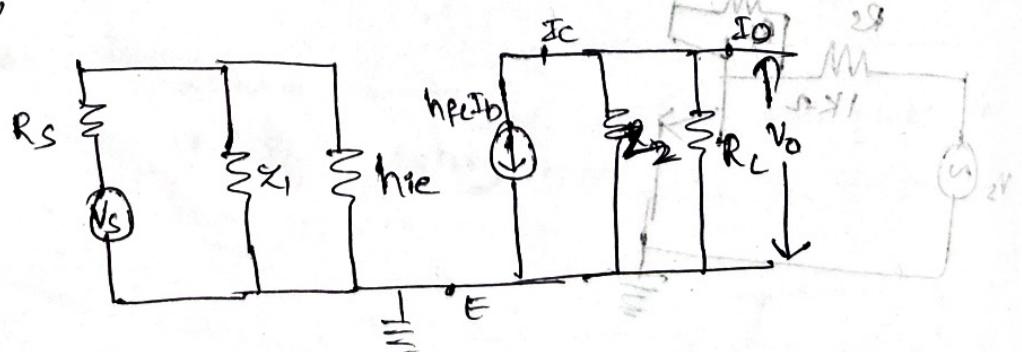

As $|h_{oe} = 0|$; we can use approximate analysis

$$A_f = -\frac{h_{fe}}{1 + h_{fe}R_s}$$

$$A_f = -h_{fe} = -50$$

$$R_i = h_{ie} = 1.1K$$

$$AV = h_{fe} \cdot \frac{R_L}{h_{ie}} = \frac{50 \times 10K}{1.1K} = 454.54$$

$$\frac{500}{1.1} = \frac{5000}{11} = 454.54$$

$$AV = -454.54 = K$$

$$R_o = 0\Omega$$

$$AV_s = AV \times \frac{Z_1}{R_s + Z_1}$$

$$= -454.54$$

$$AV_s = \frac{V_o}{V_s} \times \frac{V_p}{V_s}$$

$$AV_s = AV \times \frac{R'_i}{R'_i + R_s}$$

$$AV_s = -454.54 \times \frac{313.78}{313.78 + 1K}$$

$$AV_s = -108.56$$

$$R'_i = 411R_i$$

$$Z = \frac{X}{1-K}$$

$$= \frac{200}{1+454.54}$$

$$Z_1 = 439.02 \Omega$$

$$R'_i = 439.02 \times 1.1K$$

$$(1.1K + 439.02)$$

$$R'_i = 313.78 \Omega$$

$$A_{IS} = \frac{I_o}{I_s} = \frac{I_o}{I_c} \times \left(\frac{I_c}{I_b} \right) \times \frac{I_b}{I_s}$$

$$= \frac{A_I \times R_s}{R_L + Z_2} \quad A_I \quad \downarrow \quad \frac{Z_2}{R_L + Z_2} \quad \downarrow \quad \frac{Z_1}{Z_1 + R_s}$$

$$\therefore A_{IS} = \frac{Z_2}{R_L + Z_2} \times A_I \times \frac{R_s}{R'_i + R_s}$$

$$= \frac{200K}{10K + 200K} \times 50 \times \frac{1K}{313.78 + 1K}$$

$$\approx 0.952 \times -50 \times 0.7611$$

$$A_{IS} = -36.22$$

$$R'_o = R_{L1} \| R_{L2} \quad | R'_o = \infty \| R_L \| z_2$$

$$R'_o = R_{L1} \| R_{L2} = R_L \| z_2$$

$$= 10k \| 200k$$

$$R'_o = 9523.8 \Omega$$

$$R'_o = 9.5k\Omega$$

High Input Resistance Transistor Circuits:

Darlington Pair:


The input impedance of the CC amplifier is high but bcoz of biasing resistors, where,

$$R'_i \| R_1 \| R_2$$

the input impedance becomes

significantly less. This can be improved by direct coupling of 2 emitter follower amplifier stages.

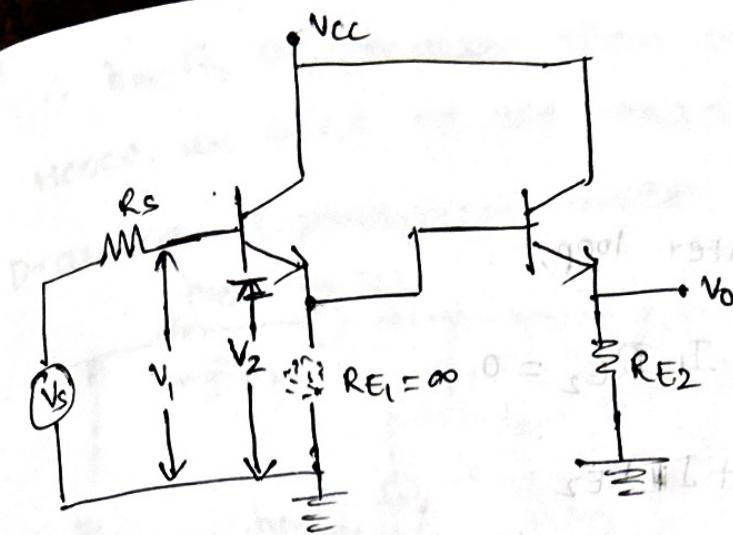* the cascaded connection of 2 emitter followers is called darlington connection / darlington pair.




Assume that, the load resistance (R_L) is such that,

$$\text{now } R_L \ll 0.1$$

Hence, we use approximate model for analyzing the 2nd stage.

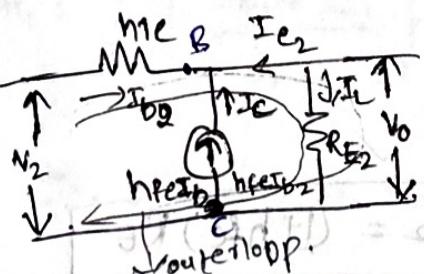The H-parameter model for 2nd stage is given as



$$A_{12} = \frac{I_L}{I_{b2}} = -\frac{I_{e2}}{I_{b2}} \quad [I_e = I_b + I_c]$$

$$= -\frac{[I_b + I_c]}{I_{b2}}$$

$$= -\frac{[I_b + h_{fe}I_b]}{I_{b2}}$$

$$= -[h_{fe} + 1]$$

$$A_{12} = 1 + h_{fe}$$

$$R_{i2} = \frac{V_2}{I_{b2}}$$

Apply KVL to outer loop:

$$V_2 - h_{ie} I_{b2} - I_L R_{E2} = 0$$

$$V_2 = h_{ie} I_{b2} + I_L R_{E2}$$

Dividing both sides by I_{b2}

$$\frac{V_2}{I_{b2}} = h_{ie} + \frac{I_L}{I_{b2}} R_{E2}$$

$$R_{E2} = R_E \because R_{E1} = \infty$$

$$R_{i2} = h_{ie} + A_{12} R_E$$

$$R_{i2} = h_{ie} + (1+h_{fe}) R_E$$

$$R_{i2} = h_{ie} + (1+h_{fe}) R_E$$

As $h_{ie} \ll (1+h_{fe}) R_E$;

$$R_{i2} = (1+h_{fe}) R_E$$

So


Darlington

Amplifier:

(Two stage CE)

Emitter follower

Circuits.

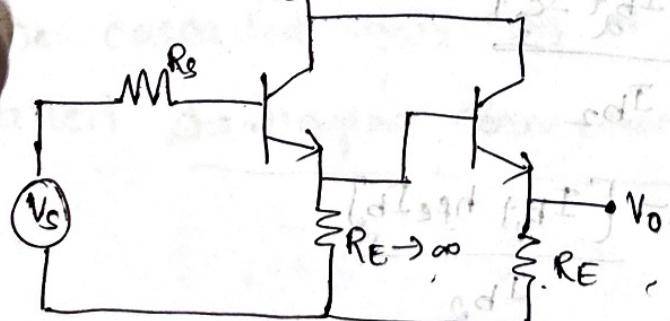


Analysis of 1st stage,

The load resistance of 1st stage is input resistance of the second stage which is R_{i2} . Generally, R_{i2} is very high.

\therefore since R_{L2} is greater than 0.1 kΩ, we need to use exact analysis.
Hence, we need to use exact analysis.

Drawing H-parameter model for 1st stage.

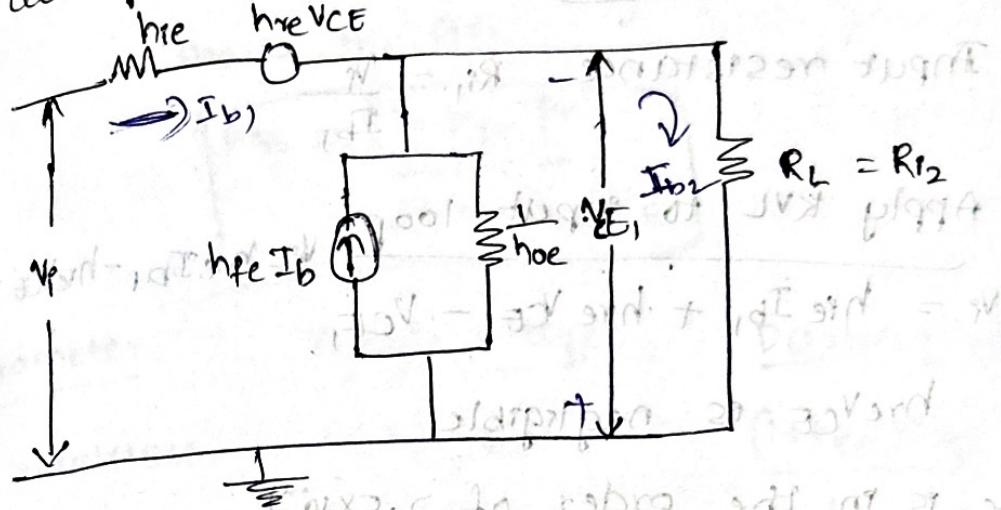

$$A_1 = \frac{I_{e1}}{I_{b1}} = \frac{I_{e1}}{I_{b1}}$$

$$A_1 = - \left[\frac{I_{b1} + I_{c1}}{I_{b1}} \right]$$

$$I_{c1} = h_{fe} I_{b1} + h_{oe} V_{CE1}$$

$$V_{CE1} = I_{b1} R_L$$

$$I_{c1} = h_{fe} I_{b1} + h_{oe} (-I_{b2}, R_4)$$

$$= h_{fe} I_{b1} + h_{oe} \cdot I_{e1} R_L$$

$$I_{e1} = -(I_{b1} + h_{fe} I_{b1} + h_{oe} I_{e1}, R_4)$$

$$I_{e1} (1 + h_{oe} R_4) = -I_{b1} (1 + h_{fe})$$

$$A_1 = - \frac{I_{e1}}{I_{b1}} = \frac{1 + h_{fe}}{1 + h_{oe} R_L}$$

$$\boxed{A_1 = \frac{1 + h_{fe}}{1 + h_{oe}(1 + h_{fe}) R_L}}$$

$$A_{V1} = \frac{1+h_{FE}}{1+h_{FE}h_{RE}}$$

$$\text{Input resistance } R_{I1} = \frac{V_p}{I_{b1}}$$

Apply KVL to input loop

$$V_i = h_{FE} I_{b1} + h_{RE} V_{CE1} - V_{CE1}$$

$h_{RE} V_{CE1}$ is negligible

h_{FE} is in the order of 2.5×10^4

$$\therefore V_i \text{ can be written as } \frac{V_i}{I_{b1}} = \frac{V_p}{I_{b1}} = \beta A$$

$$V_i = h_{FE} I_{b1} - V_{CE1}$$

$$V_{CE1} = I_{b1} R_L$$

$$I_{b2} = I_{C1}$$

$$\therefore V_i = h_{FE} I_{b1} + I_{C1} R_L$$

Dividing on both sides by I_{b1} ,

$$\frac{V_i}{I_{b1}} = h_{FE} + \frac{I_{C1}}{I_{b1}} R_L$$

$$R_{I1} = h_{FE} + A_{V1} R_L$$

$$R_{I1} = h_{FE} + A_{V1} (1+h_{FE}) R_E$$

Sub A_{V1} , we get,

$$R_{I1} = h_{FE} + \frac{(1+h_{FE})}{1+h_{FE}h_{RE}} \cdot (1+h_{FE}) R_E$$

As h_{FE} is very small compared with 2nd term.

$$R_{11} = \frac{(1+h_{fe})^2 \cdot R_E}{1+h_{oe}h_{fe}R_E}$$

The overall current gain

$$A_{1C} = A_{11} \cdot A_{12}$$

$$A_{1S} = \frac{(1+h_{fe})^2}{1+h_{oe}h_{fe}R_E}$$

Parameter

single stage

Darlington

I_P resistance

$$(1+h_{fe})R_E$$

$$= 168.3 \text{ k}\Omega$$

current gain

$$1+h_{fe}$$

(5)

$$(1+h_{fe})^2 \cdot R_E$$

$$1+h_{oe}(1+h_{fe})R_E$$

$$\frac{(1+h_{fe})^2}{1+h_{oe}h_{fe}R_E}$$

500

2) If $R_i = 3.3\text{K}$, $h_{ie} = 1100$, $h_{oe} = 2.5 \times 10^{-4}$, $h_{fe} = 50$,
 $h_{oc} = 25\text{mA/V}$

single

Darlington

I_P resistance

$$168.3 \text{ k}\Omega$$

$$1.648 \text{ M}\Omega$$

A_i

$$499.47 \approx 500$$

With this arrangement it is clear that this connection improved input impedance as well as current gain of the circuit.

Overall voltage gain,

$$Av_1 = A_{i1} \cdot \frac{R_L}{R_{i1}}, \quad Av_2 = A_{i2} \cdot \frac{R_L}{R_{i2}}$$

considering second stage Av_2 ,

$$1 - Av_2 = 1 - A_{i2} \cdot \frac{R_L}{R_{i2}}$$

$$1 - Av_2 = R_{i2} - A_{i2} \cdot R_L$$

$$\text{so } R_{i2} = \frac{R_{i2} - A_{i2} \cdot R_L}{1 - Av_2}$$

we know,

$$R_{i2} = h_{ie} + A_{i2} \cdot R_L$$

$$1 - Av_2 = \frac{R_{i2} - A_{i2} \cdot R_L}{R_{i2}}$$

$$\Rightarrow 1 - Av_2 = \frac{h_{ie} + A_{i2} \cdot R_L - A_{i2} \cdot R_L}{R_{i2}}$$

$$1 - Av_2 = \frac{h_{ie}}{R_{i2}}$$

$$Av_2 = 1 - \frac{h_{ie}}{R_{i2}}$$

$$\text{Similarly, } Av_1 = A_{i1} \cdot \frac{R_L}{R_{i1}}$$

$$1 - Av_1 = 1 - \frac{A_{i1} \cdot R_L}{R_{i1}}$$

$$1 - Av_1 = \frac{R_{i1} - A_{i1} \cdot R_L}{R_{i1}}$$

we know, $R_{i1} = h_{ie} + A_{i1} \cdot R_L$

$$1 - Av_1 = \frac{h_{ie} + A_{i1} \cdot R_L - A_{i1} \cdot R_L}{R_{i1}}$$

$$AV_1 = 1 - \frac{h_{ie}}{R_{11}}$$

$$AV_s = AV_1 \cdot AV_2$$

$$= \left(1 - \frac{h_{ie}}{R_{11}} \right) \left(1 - \frac{h_{ie}}{R_{12}} \right)$$

As R_{11} & R_{12} are very large, then

$$\frac{h_{ie}}{R_{11}}, \frac{h_{ie}}{R_{12}} \text{ becomes very small}$$

Then, the overall voltage gain AV_s approaches 1.

Output impedance, R_{O2}

$$Y_O = h_{oc} - \frac{h_{fe} \cdot h_{re}}{h_{re} + R_S}$$

$$h_{re} = 1, h_{ic} = h_{re}, h_{oc} = h_{oe}$$

$$h_{fe} = -(1 + h_{fe})$$

$$Y_{O1} = \frac{h_{oe} + (1 + h_{fe})}{h_{re} + R_S}$$

$$Y_{O1} = 1 + h_{fe}$$

$$h_{re} + R_S$$

$$R_{O1} = \frac{h_{re} + R_S}{1 + h_{fe}}$$

R_{O1} of the 1st stage is the source resistance of the 2nd stage.

$$\therefore R_{O1} = R_{S2}$$

$$\therefore R_{O2} = \frac{R_S + h_{ie2}}{1+h_{fe}}$$

$$\therefore R_{O2} = \left(\frac{h_{ie1} + R_S}{1+h_{fe}} \right) + h_{ie2}$$

$$R_{O2} = \frac{h_{ie1} + R_S + h_{ie2}(1+h_{fe})}{(1+h_{fe})^2}$$

$$R_{O2} = \frac{h_{ie1} + R_S + h_{ie2}}{(1+h_{fe})^2} + \frac{h_{ie2}}{(1+h_{fe})}$$

\Rightarrow As current in t_2 is $(1+h_{fe})$ times the current in t_1 .

$$h_{ie1} = (1+h_{fe}) h_{ie2}$$

$$\Rightarrow R_{O2} = \frac{R_S}{(1+h_{fe})^2} + \frac{2h_{ie2}}{1+h_{fe}}$$

\Rightarrow H-parameters of t_1 & t_2 are identical.

* Cascading of n-stages is not possible in darlington pair bcoz, i) the ac o/p of 1st stage is $(1+h_{fe}) I_B$

If n-stages are considered then the o/p current would be amplified by $(1+h_{fe})^n I_B$

providing, a very high current gain which may have the power stage which is not required for the amplifier circuits.




(ii) The leakage current is the 1st transistor's

amplified by the 2nd transistor, increasing the overall leakage current which is not desirable.

Q: For a ckt. of a darlington amplifier calculate

g: For a ckt. of a darlington amplifier calculate
 R_s , A_V , and R_o given, $h_{ie} = 1.1 K$, $h_{fe} = 50$,

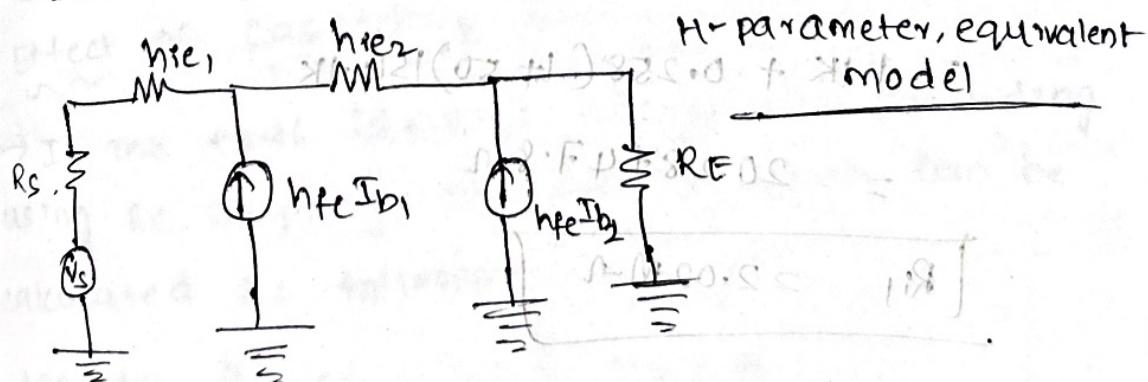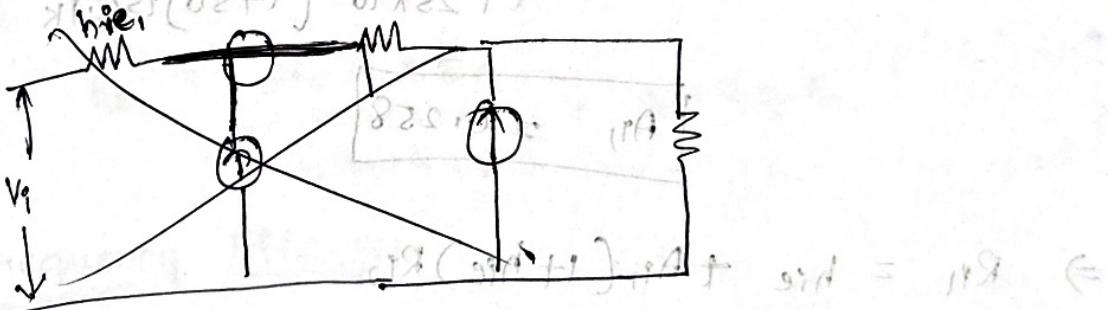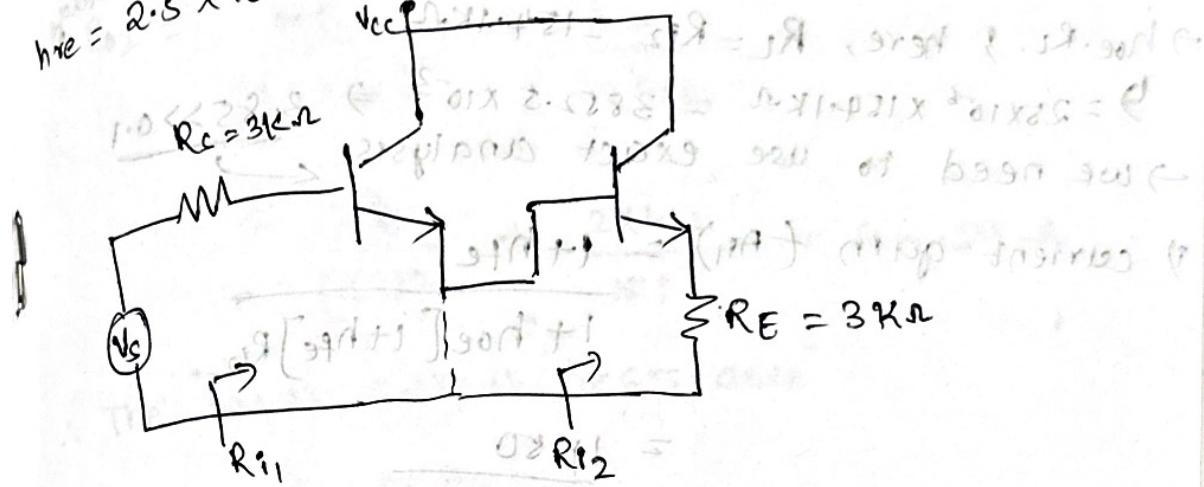$h_{oe} = 2.5 \times 10^{-4}$, $h_{re} = 25 \mu A/V$, $R_s = 3 K\Omega$, $R_c = 3 K\Omega$



approximate V_A
 $\Rightarrow h_{oe} \cdot R_L < 0.1 \Rightarrow$ cond'n for exact analysis.

$$(25 \times 10^{-6} \times 3 \times 10^3) < 0.1$$

$$0.075 < 0.1$$

\therefore we need to go for approximate analysis.

Approximate analysis of 2nd stage:

$$R_2 = \frac{(1+h_{fe}) R_E}{h_{re}} = \frac{1+50 \times 3}{25 \times 10^{-6}} = 154.1 K\Omega$$

$$A_{12} = 1 + h_{fe}$$

$$A_{12} = 1 + 50 = 51$$

$$Av_2 = \frac{1 - h_{ie}}{R_{12}} \approx 1 - \frac{1.1K}{153K} = 0.993$$

$$R_{12} = h_{ie} + (h_{fe} + 1)RE = 1.1K + (51)3K = 154.1K$$

Analyses of 1st stage:

R_2 of 1st stage is input impedance of 2nd stage
 $\Rightarrow h_{oe} \cdot R_L$. But here, $R_L = R_{12} = 154.1K$

$$b = 25 \times 10^6 \times 154.1K = 3852.5 \times 10^3 \Rightarrow 3.85 > 0.1$$

\rightarrow we need to use exact analysis.

$$\text{i) current gain } (A_{11}) = \frac{1 + h_{fe}}{1 + h_{oe}(1 + h_{fe})R_{12}}$$

$$= \frac{1 + 50}{1 + 25 \times 10^6 [1 + 50] 154.1K}$$

$$A_{11} = 0.258$$

$$\Rightarrow R_{11} = h_{ie} + A_{11}(1 + h_{fe})R_{12}$$

~~$$1.1K + 0.258(1 + 50)154.1K$$~~

~~$$= 202.8 + 47.8K$$~~

$$R_{11} = 2.02M\Omega$$

$$Av_1 = 1 - \frac{h_{ie}}{R_{11}}$$

$$= 1 - \frac{1.1K}{2.02M} = 0.99$$

$$Av_s = Av_1 \cdot Av_2$$

$$= (0.99)(0.99) \approx 0.9904 \approx 0.980$$

$$Av_s = 0.9801$$

$$R_{O1} = \frac{R_S + h_{FE}}{1+h_{FE}}$$

$$= \frac{3K + 1.1K}{1+50} = \frac{4.1K}{51} = 80.39\Omega$$

$$R_{O2} = \frac{R_S}{(1+h_{FE})^2} + \frac{2h_{FE}}{1+h_{FE}}$$

$$= \frac{3K}{(51)^2} + \frac{2 \times 1.1K}{51} = 44.29\Omega$$

\therefore The total output resistance

$$R_O = R_{O2} || R_E$$

$$R_O = \frac{44.29 \times 3K}{44.29 + 3K} = 43.64\Omega$$

frequency Effects:

Effect of cascading on Gain:

→ If the no. of identical stages are cascading using RC coupling, the overall gain can be calculated as follows,

$$\text{consider } A_{mid(\text{overall})} = \left| \frac{A_{mid}}{1 + \left(\frac{f_L}{f} \right)^2} \right|^n$$

for a single stage,

$$\left| \frac{A_L}{A_{mid}} \right| = \sqrt{1 + \left(\frac{f_L}{f} \right)^2} \quad \Rightarrow \text{for a single stage}$$

then the overall low frequency gain will be

$$\left| \frac{A_L}{A_{mid}} \right|^n = \frac{1}{\sqrt{1 + \left(\frac{f_L}{f} \right)^2} + 1}$$

The lower 3dB frequency for overall low frequency gain can be defined at $f = f_L$.

$$\left| \frac{A_L}{A_{mid}} \right|^n = \frac{1}{\sqrt{1 + \left(\frac{f_L}{f} \right)^2}} = \left[1 + \left(\frac{f_L}{f} \right)^2 \right]^{n/2}$$

$$f = f_L \Rightarrow \boxed{\left| \frac{A_L}{A_{mid}} \right|^n = \frac{1}{\sqrt{2}}}$$

for n -stages,

$$\boxed{\left| \frac{A_L}{A_{mid}} \right|^n = \left[1 + \left(\frac{f_{L(n)}}{f_L} \right)^2 \right]^{n/2}}$$

Similarly, the overall high frequency gain is,

$$\boxed{\left| \frac{A_H}{A_{mid}} \right|^n = \frac{1}{\sqrt{2}} = \left[1 + \left(\frac{f_{H(n)}}{f_H} \right)^2 \right]^{n/2}}$$

Then the gain of multistage amplifier at any frequency below the cutoff frequency of individual stage is given as

$$\boxed{A_V = \left(A_{Vmid} \right)^n \left[1 + \left(\frac{f_L}{f} \right)^2 \right]^{n/2}}$$

Similarly, the gain of the multistage amplifier at any frequency above higher cutoff frequency of individual stage is

$$\boxed{A_V = \left(A_{Vmid} \right)^n \left[1 + \left(\frac{f}{f_H} \right)^2 \right]^{n/2}}$$

Q: A multistage amplifier with 4 identical stages each of which has a lower cutoff frequency of 20Hz & upper cutoff frequency of 20KHz. calculate the gain of multistage amplifier at 4.5Hz and at 200KHz. Assume mid band voltage gain of each stage is 10.

$$AV_1 = \frac{(10)^4}{\left[1 + \left(\frac{20}{4.5}\right)^2\right]^2}$$

$$AV_1 = 151.998$$

$$AV_2 = \frac{(10)^4}{\left[1 + \left(\frac{200K}{20K}\right)^2\right]^2}$$

$$AV_2 = 0.9802$$

Effect of cascading on Bandwidth:
The bandwidth of cascading amplifier is always less than that of BW of single stage amplifier.
consider a lower 3dB frequency of n-identical cascading stage. $f_L(n)$

$$\frac{1}{\left[1 + \left(\frac{f_L}{f_L(n)}\right)^2\right]^{n/2}} = \frac{1}{\sqrt{2}}$$

S.O.B.S

$$\left[1 + \left(\frac{f_L}{f_L(n)}\right)^2\right]^n = 2$$

Taking n th root on both sides,

$$(2)^{1/n} = 1 + \left(\frac{f_L}{f_{L(n)}}\right)^2$$

$$\text{band by } 2^{1/n} - 1 = \left[\frac{f_L}{f_{L(n)}}\right]^2$$

$$\therefore \left(\frac{f_{L(n)}}{f_L}\right)^2 = \frac{2^{1/n} - 1}{1}$$

$$\left(f_{L(n)}\right)^2 = \frac{(f_L)^2}{2^{1/n} - 1}$$

$$\left(\frac{f_{L(n)}}{f_L}\right) = \sqrt{\frac{2^{1/n} - 1}{(f_L)^2}}$$

$$f_{L(n)} = f_L \sqrt{\frac{2^{1/n} - 1}{(f_L)^2}}$$

Upper 3dB frequency: high frequency decreases

$$\frac{1}{\sqrt{2}} = \frac{1}{\left[1 + \left(\frac{f_{H(n)}}{f_H}\right)^2\right]^{1/2}}$$

$$\sqrt{2} = \left[1 + \left(\frac{f_{H(n)}}{f_H}\right)^2\right]^{1/2}$$

$$2 = \left[1 + \left(\frac{f_{H(n)}}{f_H}\right)^2\right]$$

$$2^{1/n} - 1 = \left(\frac{f_{H(n)}}{f_H}\right)^2$$

$$\left[\sqrt{2^{1/n} - 1}\right] f_H = f_{H(n)} \cdot 2$$

$$f_{H(n)} = \left[\sqrt{2^{1/n} - 1} + 1\right] f_H$$

increases